

## **Design Assignment 2**

Zurizadae Soto Maya [1010229548]

Zarah Mathew [1009961720]

October 12, 2025

## **I. Updated Schematic**

### **Design Changes Summary**

#### **1. Current Sense Amplifier (DA1)**

No design changes were made as it was approved and validated by our instructor.

#### **2. Low-Pass Filter**

A 4th-order Butterworth Bessel 0.95 filter implemented using two cascaded op-amps. This type of filter is used to achieve smooth roll-off and minimal phase distortion.

- Gain: 0 dB
- Cutoff Frequency: 1kHz (-0.399 dB at cutoff) ( $\approx 0$ dB)
- Stopband Frequency: 5kHz with -43 dB attenuation ( $\leq -35$ dB).
- Resistors:  $9\text{k}\Omega$ ,  $38.6\text{k}\Omega$ ,  $5.71\text{k}\Omega$ ,  $11.2\text{k}\Omega$
- Capacitors:  $1.8\text{nF}$ ,  $18\text{nF}$ ,  $12\text{nF}$ ,  $15\text{nF}$

Attached below is the updated schematic. Resistor and capacitor values are adjusted to the nearest standard values accordingly.

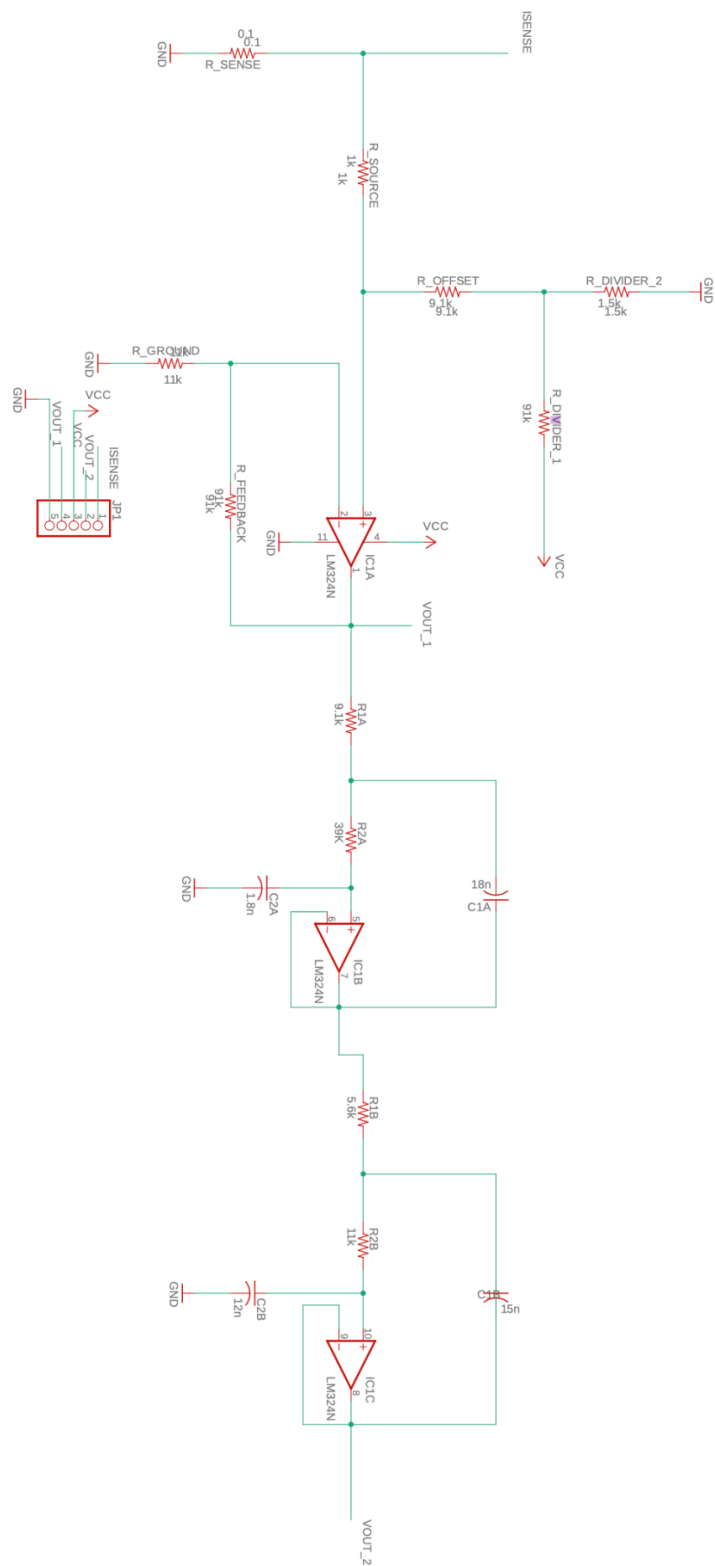


Figure 1: Updated Schematic

II. PCB Layout


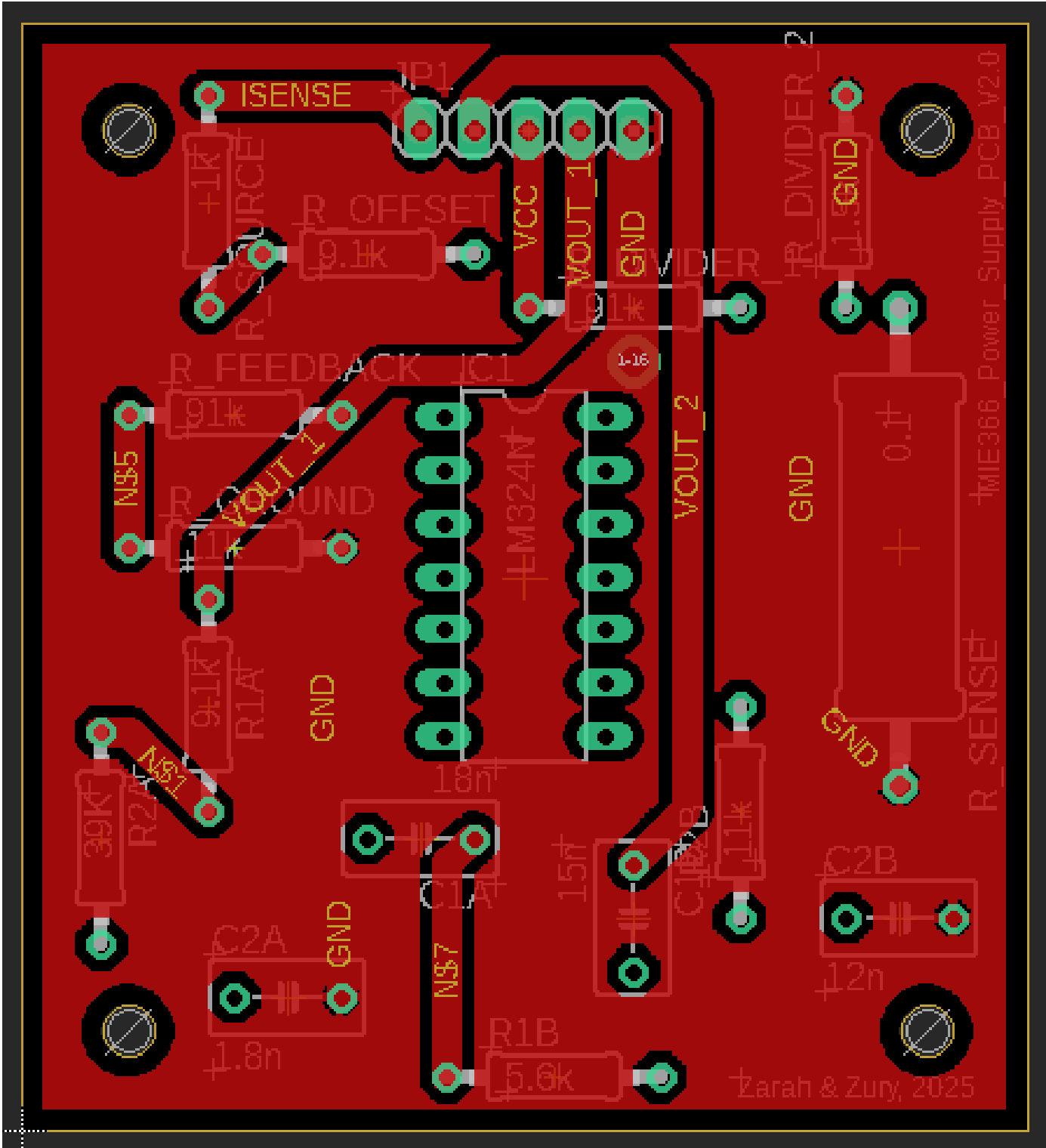


Figure 2: Updated Top Component Layer

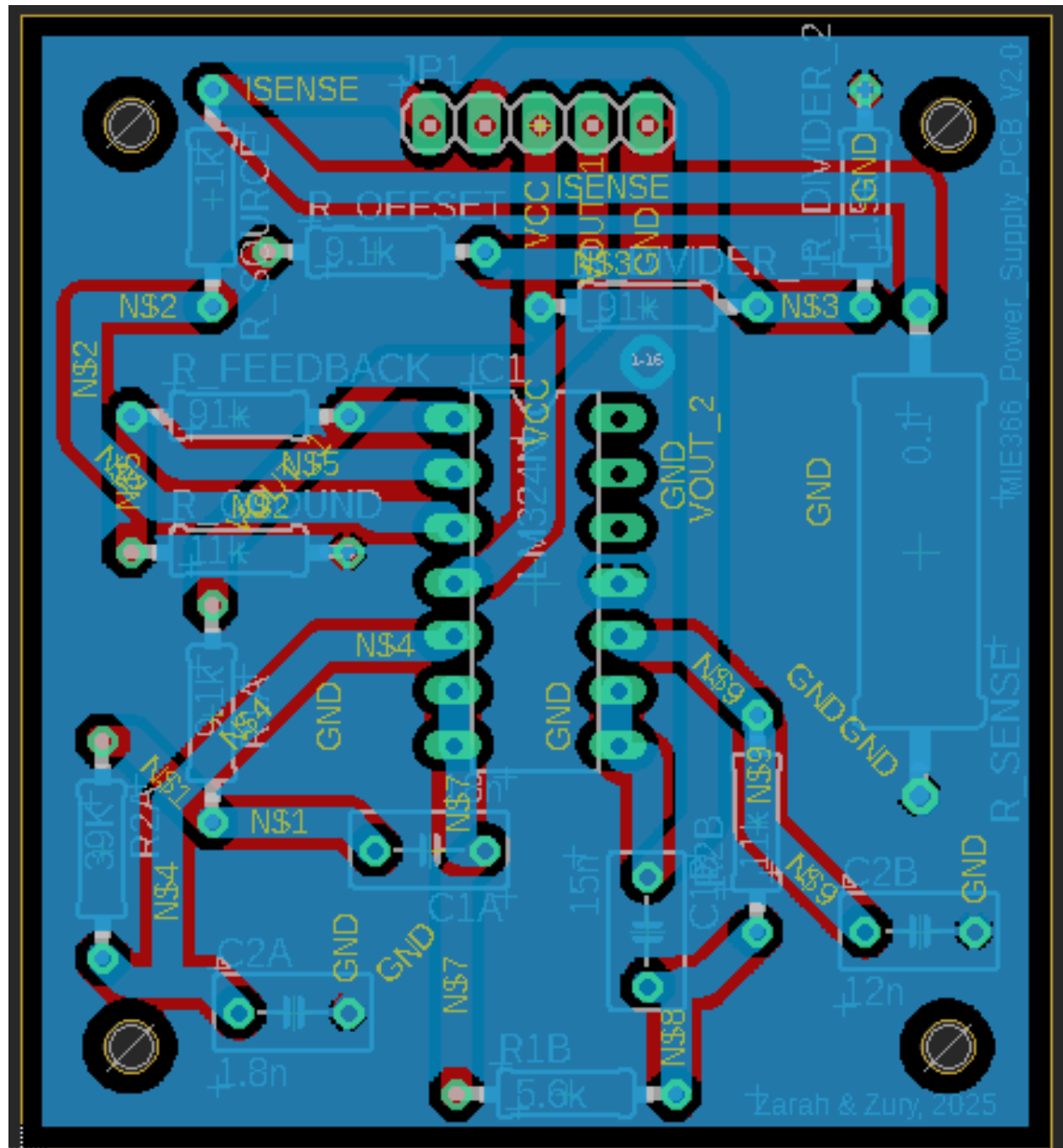

### Figure 3: Updated Bottom Soldering Layer



**Figure 4: Updated Combined Top and Bottom Layer**